

CMPT 295

Assignment 4: CPU CIRCUIT SUBMITTED: MARCH 23rd, 2016

1. Wong, Ivan, 301219319, icwong@sfu.ca
2. Dai, Marcus, 301243340, zdai@sfu.ca

TABLE OF CONTENTS

1. Documentation File Index:
 - a. a4solns.pdf: Solution to assignment questions
 - b. circuit.pdf: CPU Circuit with CM component

2. Complete the following table, listing all the μ -instructions and their corresponding control words that this CPU is capable of performing.

| # | INSTRUCTIONS | CONTROL WORDS | | | | |
|----|--|---------------|----|----|----|----|
| | | Cl | lb | la | s0 | oe |
| 1 | $A \leftarrow \text{DATA INPUT}$ | 0 | 0 | 1 | 1 | 0 |
| 2 | $B \leftarrow \text{DATA INPUT}$ | 0 | 1 | 0 | 1 | 0 |
| 3 | $B \leftarrow A+B$ / $\text{DATA OUTPUT} \leftarrow A+B$ | 0 | 1 | 0 | 0 | 0 |
| 4 | $B \leftarrow A+B+1$ / $\text{DATA OUTPUT} \leftarrow A+B+1$ | 1 | 1 | 0 | 0 | 0 |
| 5 | $A \leftarrow A+B$ | 0 | 0 | 1 | 0 | 0 |
| 6 | $A \leftarrow A+B+1$ | 1 | 0 | 1 | 0 | 0 |
| 7 | $A,B \leftarrow \text{DATA INPUT}$ | 0 | 1 | 1 | 1 | 0 |
| 8 | $A,B \leftarrow A+B$ | 0 | 1 | 1 | 0 | 0 |
| 9 | $A,B \leftarrow A+B+1$ | 1 | 1 | 1 | 0 | 0 |
| 10 | $\text{DATA OUTPUT} = B$ | 0 | 0 | 0 | 0 | 0 |
| 11 | $\text{DATA OUTPUT} = Z$ (HIGH IMPEDENCE) | 0 | 0 | 0 | 0 | 1 |

3. Express the behaviour of the CM component as a function selection table.

| $\sim Cl$ | cm | Function |
|-----------|----|-------------------------------------|
| 0 | 0 | Data Output = Does not change |
| 0 | 1 | Data Output = Complement data input |
| 1 | 0 | Data Output = 0 |
| 1 | 1 | Data Output = 0 |

6. Extend your table in (2) to include the control inputs of CM and to include any additional μ -instructions that are now possible with this enhancement.

| # | INSTRUCTIONS | CONTROL WORDS | | | | | | | |
|----|---|---------------|----|----|----|---|----|----|----|
| | | Cl | lb | la | s0 | X | oe | cm | cl |
| 12 | $A \leftarrow \text{COMPLEMENT DATA INPUT} / \sim A$ | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 13 | $B \leftarrow \text{COMPLEMENT DATA INPUT} / \sim B$ | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 14 | $A \leftarrow \text{COMPLEMENT DATA INPUT}+1 / \sim A+1$ | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| 15 | $B \leftarrow \text{COMPLEMENT DATA INPUT} +1 / \sim B+1$ | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 16 | $A,B \leftarrow \text{COMPLEMENT DATA INPUT} / \sim A+\sim B$ | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 |
| 17 | $A,B \leftarrow \text{COMPLEMENT DATA INPUT}+1 / \sim A+\sim B+1$ | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 0 |
| 18 | $A \leftarrow 0$ (WITHOUT DATA INPUT) | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| | $A \leftarrow 0$ (WITHOUT DATA INPUT) | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 19 | $B \leftarrow 0$ (WITHOUT DATA INPUT) | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| | $B \leftarrow 0$ (WITHOUT DATA INPUT) | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 20 | $A,B \leftarrow 0$ (WITHOUT DATA INPUT) | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| | $A,B \leftarrow 0$ (WITHOUT DATA INPUT) | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |

7. For each of the following proposed assembly language instructions from a hypothetical instruction set architecture, provide a sequence of μ -instructions that, when executed will perform the desired instruction.

| | | | | CONTROL WORDS | | | | | | | |
|----|------|------------|--------------------------------------|---------------|----|----|----|---|----|----|----|
| | OPR | OPND | SEMANTICS | Cl | lb | la | s0 | X | oe | cm | cl |
| A) | CLR | A | $A \leftarrow 0$ | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| | | | | | | | | | | | |
| B) | INC | B | $B \leftarrow B+1$ | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| | | | | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| | | | | | | | | | | | |
| C) | SHL1 | A | $A \leftarrow A \ll 1$ | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 |
| | | | | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| | | | | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| | | | | | | | | | | | |
| D) | SET | B | $B \leftarrow 1$ | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |
| | | | | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| | | | | | | | | | | | |
| E) | DECB | DATA INPUT | $B \leftarrow B - \text{DATA INPUT}$ | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |
| | | | | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |